

TFB2093 Internet-of-Things

Practical 06 — Assignment (TinkerCAD-Only, 3 Tasks)

Goal: Practice analog sensing/actuation in **TinkerCAD Circuits (Arduino Uno)**.

Submit: One short PDF + TinkerCAD share links.

Task 1 — Potentiometer Read & Plot

Build: Pot (10 kΩ) → A0 (5V, GND, A0).

Code: Print **raw (0-1023)** and **percent (0-100%)**.

Plot: Show live signal in **Serial Plotter**.

Deliverables: - TinkerCAD link

- 1 Serial Monitor screenshot (min/mid/max) + 1 Serial Plotter screenshot

- **Reflection (2-3 lines):** What does mapping do and why is it useful?

Task 2 — LDR Voltage Divider with Thresholds

Build: 5V — LDR — **A1** — 10 kΩ — GND (A1 is the mid-node).

Code: Print raw light level and classify **Bright / Normal / Dark** with simple thresholds.

Deliverables: - TinkerCAD link

- 3 screenshots (bright, normal, dark)

- **Reflection (2-3 lines):** One limitation of LDRs and when you'd use a different sensor.

Task 3 — Servo from Potentiometer (Smooth Motion)

Build: Servo signal → **D9**, +5V, GND; Pot on A0.

Code: Map A0 to **0-180°** and add simple **rate-limit/deadband** to reduce jitter.

Deliverables: - TinkerCAD link

- 1 screenshot (servo wiring + running)

- **Reflection (2-3 lines):** Trade-off between smoothness and responsiveness.

Submission Checklist

- [] PDF named `TFB2093_P06_<ID>_<Name>.pdf`
- [] TinkerCAD **share links** (viewable without login)
- [] Short reflections included under each task
- [] Key code snippets pasted (or appendix)

Due: 12 Nov 2025, 23:59 (Asia/Kuala_Lumpur). **Integrity:** Work individually; links must be your own circuits.

Tip: If plots look noisy, try a small moving average ($N \approx 10$) or add a 20-50 ms delay in `loop()`.